

# Introduction to Computing Systems Homework 2

PB20000051 Fu Shen(fushen@mail.ustc.edu.com)

October 26, 2021

## Question 1.

---

It's  $2^{-126}$ , as 0000 0000 1000 0000 0000 0000 0000 0000 represents.

## Question 2.

---

It's  $2^{31} - 1 = 2147483647$ , as 0111 1111 1111 1111 1111 1111 1111 1111 represents.

## Question 3.

---

a. See Figure 1.

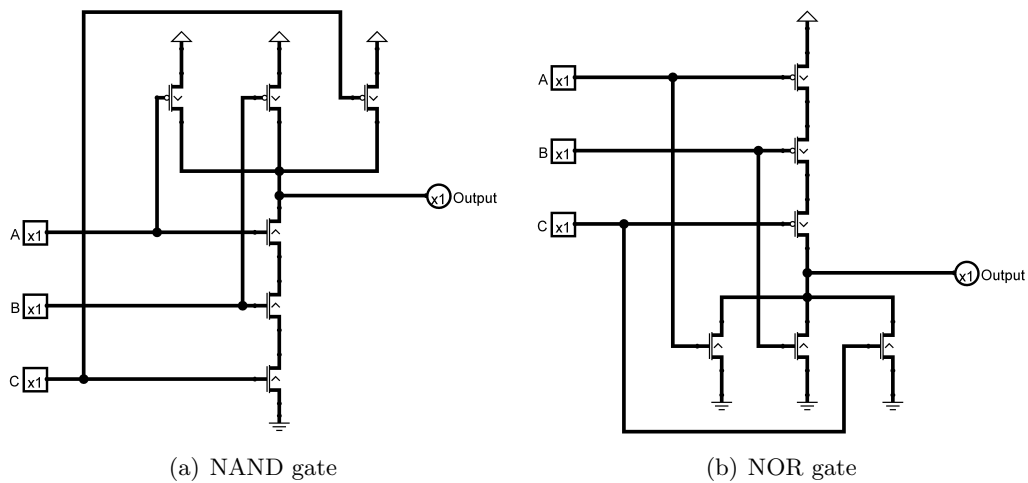


Figure 1: 3-input gate (Made by Logisim)

- b. See Figure 2. The output of NAND gate is 1 and the output of NOR gate is 0;

 


Figure 2: Circuit's operation (Made by Logisim)

- c. See Figure 3.

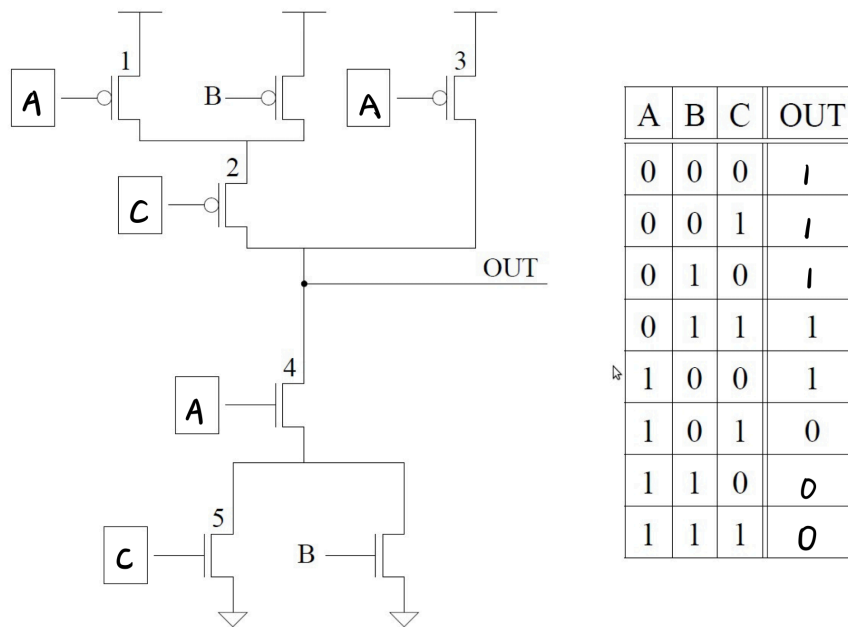


Figure 3: The answer to question 3.c

#### Question 4.

- a. X  
b. 1

c. 0

d. X

e. 0

f. 0

**Question 5.**

Logic circuit 2 involve the storage of information but logic circuit 1 do not. For example, when the voltage at input A goes from 0 to 1, the output of logic circuit 1 will go from C to B. But if the input B in logic circuit 2 is 1, the output D won't change, remaining to be 1, which is described the *quiescent* state, so the previous information is stored. And if the input B is 0, the output D will go from a uncertain state to 0. The name of logic circuit is the 2-to-1 mux, and the name of the other is the R-S latch.

**Question 6.**

6.1) See Table 1.

Table 1: Truth table of Question 6.(1)

S1	S0	A	B	C	D	OUT	S1	S0	A	B	C	D	OUT
0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	0	0	0	0	1	0	1	0	0	0	0	1	0
0	0	0	0	1	0	0	1	0	0	0	1	0	1
0	0	0	0	1	1	0	1	0	0	0	1	1	1
0	0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	1	0	1	0	0	1	0	1	0
0	0	0	1	1	0	0	1	0	0	1	1	0	1
0	0	0	1	1	1	0	1	0	0	1	1	1	1
0	0	1	0	0	0	1	1	0	1	0	0	0	0
0	0	1	0	0	1	1	1	0	1	0	0	1	0
0	0	1	0	1	0	1	1	0	1	0	1	0	1
0	0	1	0	1	1	1	1	0	1	0	1	1	1
0	0	1	1	0	0	1	1	0	1	1	0	0	0
0	0	1	1	0	1	1	1	0	1	1	1	0	1
0	0	1	1	1	0	1	1	0	1	1	1	1	1
0	1	0	0	0	0	0	1	1	0	0	0	0	0
0	1	0	0	0	1	0	1	1	0	0	0	1	1
0	1	0	0	1	0	0	1	1	0	0	1	0	0
0	1	0	0	1	1	0	1	1	0	0	1	1	1
0	1	0	1	0	0	1	1	1	0	1	0	0	0
0	1	0	1	0	1	1	1	1	0	1	0	1	1
0	1	0	1	1	0	1	1	1	0	1	1	0	0
0	1	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	0	0	0	0	1	1	1	0	0	0	0
0	1	1	0	0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	0	0	1	1	1	0	1	0	0
0	1	1	0	1	1	0	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1	1	1	1	0	0	0
0	1	1	1	0	1	1	1	1	1	1	0	1	1
0	1	1	1	1	0	1	1	1	1	1	1	0	0
0	1	1	1	1	1	1	1	1	1	1	1	1	1

**6.2)** See Figure 4(a).

**6.3)** See Figure 4(b).

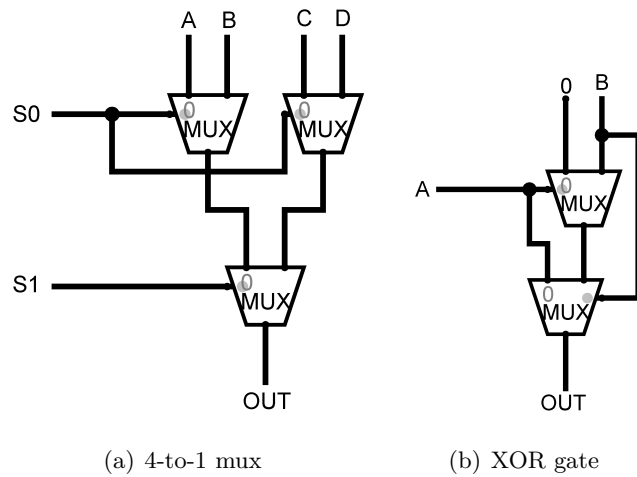


Figure 4: The implementation using 2-to-1 muxes.(Made by Logisim)

### Question 7.

- a. It's 3.
- b. It's 12.
- c. See Figure 5. Its propagation delay is 3, instead of 4 in the question figure.

 


Figure 5: A different implementation. (Made by Logisim)

### Question 8.

Just connect every condition that  $S_i/C_{i+1}$  is 1 with the corresponding OR gate. See Figure 6.

 


Figure 6: A full-adder. (Made by Logisim)

**Question 9.**

a. See Figure 7

 


Figure 7: The state diagram of the elevator scheduling

b. See Table 2. The representation of State is  $S$ , and the representation of input & output is  $In$  &  $Out$ .

Table 2: Truth table of elevator controller.

$S_1$	$S_0$	$In_1$	$In_0$	$S'_1/Out'_1$	$S'_0/Out'_0$
0	0	0	x	0	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	x	0	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	1	0
1	0	1	x	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	x	1	1

**Question 10.**

The state after 50 cycles is 111000. It takes 6 cycles for a specific state to show up again, that is

$$100000 \rightarrow 111000 \rightarrow 111110 \rightarrow 011111 \rightarrow 000111 \rightarrow 000001 \rightarrow 100000$$

**Question 11.**

See Figure 8.

 


Figure 8: 2 input XOR gate

**Question 12.**

a. See Table 3.

Table 3: The truth table for a 1-bit comparator.

A	B	G	E	L
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

b. See Figure 9(a).

c. See Figure 9(b).

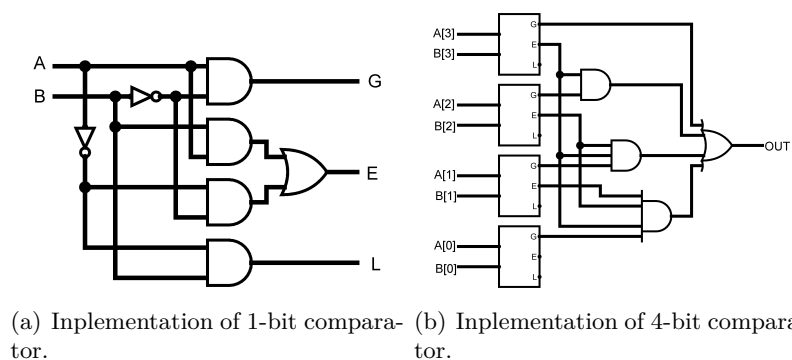


Figure 9: Comparator

**Question 13.**

See Table 4 and Figure 10.

 


Figure 10: The logic circuit for the alarm.

Table 4: The truth table for the alarm.

A	B	C	D	Z
0	x	0	0	0
0	0	1	0	0
0	0	x	1	1
0	1	0	1	0
0	1	1	x	1
1	x	0	0	0
1	x	0	1	1
1	x	1	x	1

**Question 14.**

It's obvious that

$$\text{NOT } X = X \text{ NAND } X$$

$$X \text{ AND } Y = \text{NOT } (X \text{ NAND } Y) = (X \text{ NAND } Y) \text{ NAND } (X \text{ NAND } Y)$$

$$X \text{ OR } Y = (\text{NOT } X) \text{ NAND } (\text{NOT } Y) = (X \text{ NAND } X) \text{ NAND } (Y \text{ NAND } Y)$$

And because the set of gates  $\{\text{AND}, \text{OR}, \text{NOT}\}$  is logically complete, NAND is logically complete.